

Beth rydyn ni'n mynd i ddysgu heddiw?

- Ddylai rhai ohonych gallu gwneud hyn:

Draw circuit symbols

- Ddylai mwyafrif ohonych gallu gwneud hyn:

Construct a simple circuit

- Ddylai pob un ohonych gallu gwneud hyn:

Explain the operation of a simple circuit using key terms (current, charge & voltage)