

Answers written by amonversis

PAGNale

Q 1


- i)
1. AND GATE
  2. OR GATE
  3. X OR GATE
  - 4.
  5. NOR

2/5

ii)


0/5

iii)

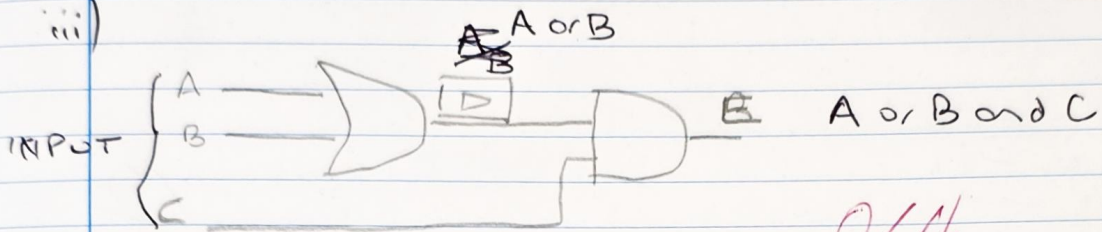

0/4

iv)

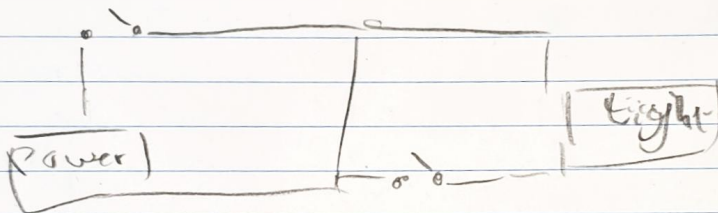

Power

LIGHT

3/6 5/6